

# **Lab 3: Multiplier with Control Unit Design Using VHDL**

ENGG3050: Reconfigurable Computing Systems

**Instructor:**  
Dr. Shawki Areibi

**Group 42: Tuesday-3:30 Section**

**Bilal Ayyache: 0988616**  
**Anthony Granic: 0994824**

**Lab Start Date:** October 3, 2019

**Lab End Date:** October 8, 2019

# Contents

<b>1</b>	<b>Project Implementation</b>	<b>1</b>
1.1	Problem Statement . . . . .	1
1.2	Assumptions and Constraints . . . . .	1
1.3	System Overview Justification Of Design . . . . .	1
1.3.1	Designed System Overview . . . . .	1
1.3.2	System Functionality and Reasons Behind Design . . . . .	1
1.4	System design diagrams . . . . .	2
<b>2</b>	<b>Software Implementation (VHDL)</b>	<b>4</b>
2.1	Top-Level Module . . . . .	5
2.2	7-Segment Display . . . . .	6
2.3	Multiplier . . . . .	8
2.4	Control Unit . . . . .	9
2.5	Registers . . . . .	11
2.6	Component Package . . . . .	12
2.7	Bench Test . . . . .	13
2.8	Top ALU . . . . .	16
2.9	ALU . . . . .	17
2.10	Full Adder . . . . .	19
2.11	Half Adder . . . . .	20
2.12	XDC . . . . .	20
<b>3</b>	<b>Hardware Overview</b>	<b>23</b>
3.1	Hardware Implementation . . . . .	23
3.2	Hardware Schematic . . . . .	23
3.3	Resources Used . . . . .	27
<b>4</b>	<b>Project Development Process</b>	<b>29</b>
4.1	Error Analysis . . . . .	29
4.2	Simulation Analysis . . . . .	29
4.2.1	Results Analysis . . . . .	29
4.2.2	Simulation Figures . . . . .	29

# List of Figures

1	State Diagram . . . . .	2
2	Meele Machine . . . . .	3
3	Stages counter . . . . .	3

4	System Outputs . . . . .	4
5	Stages overview . . . . .	4
6	Schematic of the top level module . . . . .	23
7	Schematic of the seven segment driver-1 . . . . .	23
8	Schematic of the seven segment driver-2 . . . . .	24
9	Multiplier Hardware Overview . . . . .	24
10	Control Unit Implementation-1 . . . . .	25
11	Control Unit Implementation-2 . . . . .	25
12	Registers Implementation . . . . .	26
13	Resources used summary . . . . .	27
14	Resources Used from FPGA Board . . . . .	27
15	Hardware Usage(Detailed View) . . . . .	28
16	Hardware Usage(Zoomed In View) . . . . .	28
17	Structural Implementation Results . . . . .	29
18	Behavioral Implementation Results . . . . .	30
19	Structural vs Behavioral Comparison . . . . .	30
20	Structural Implementation Test 1 . . . . .	30
21	Structural Implementation Test 2 . . . . .	30

## List of Tables

1	Example of multiplier behaviour . . . . .	1
---	---	---

# 1 Project Implementation

## 1.1 Problem Statement

The main objective of lab 3 is to design and implement a multiplier that can multiply two 4-bit unsigned binary numbers using Structural VHDL.

## 1.2 Assumptions and Constraints

Constraints includes using an FPGA board, programming in VHDL, and testing project using Vivado as a design tool. Design must be mapped successfully on the FPGA board with no errors. VHDL code must be structural and not behavioral (for most parts). It was also assumed that the FPGA board was fully functional.

## 1.3 System Overview Justification Of Design

The system made incorporates a decoder based control unit to decide which stage of standard serial multiplication the system is at. After 32 iterations the program stops and displays the output. This method of multiplication incorporates multiple shift registers and an ALU to add the shifted values of the numbers together.

### 1.3.1 Designed System Overview

The final design incorporates 3 shift registers, an ALU (only adding is used), and a control unit. The final design has the desired output of the product of two unsigned 4-bit numbers displayed in a hexadecimal format.

A (binary)	B (binary)	Product (hex)
0100	0011	0C
1010	0100	28
0010	1111	20

Table 1: Example of multiplier behaviour

### 1.3.2 System Functionality and Reasons Behind Design

The system operates based on the decisions of the control unit. The control unit decides when the system should add, load, shift, or wait based on the current state of the least significant bit of the product or the iteration counter. The registers receive these signals and shift or output based on the signal received. Once the iteration counter reaches 32 the program waits for the next time it needs to multiply the operands.

This system has two 4-bit inputs that represent unsigned numbers. This was done using 8 switches. These inputs and the 8-bit output were mapped to a seven segment display to be represented as hexadecimal

values. A button on the board initiates the multiplication of the currently inputted values. An LED is used to indicate the completion of multiplication.

This design was an efficient way to implement a serial multiplier and allowed complete control of when the operands were to be multiplied. This reduced error in the display of the hexadecimal values on the seven segment display as intermediate values were not displayed or multiplied.

### 1.4 System design diagrams

The design of this system was based off of these diagrams referenced from chapter 3.5 of Computer Organization and Design 5th edition by David A. Patterson and John L. Hennessy.

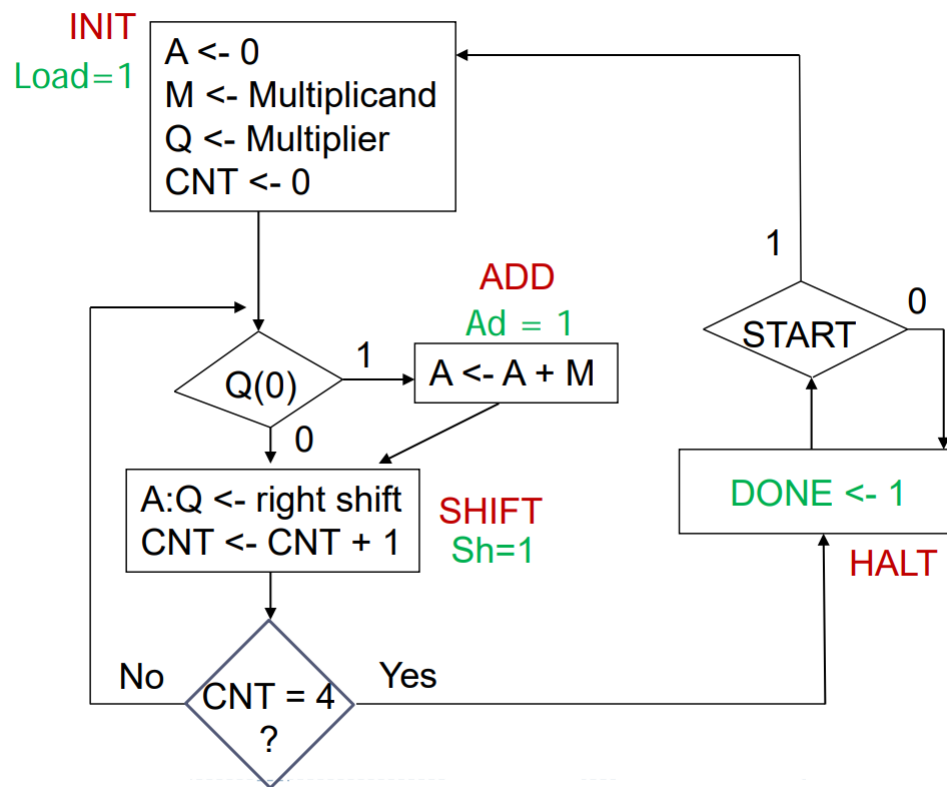


Figure 1: State Diagram

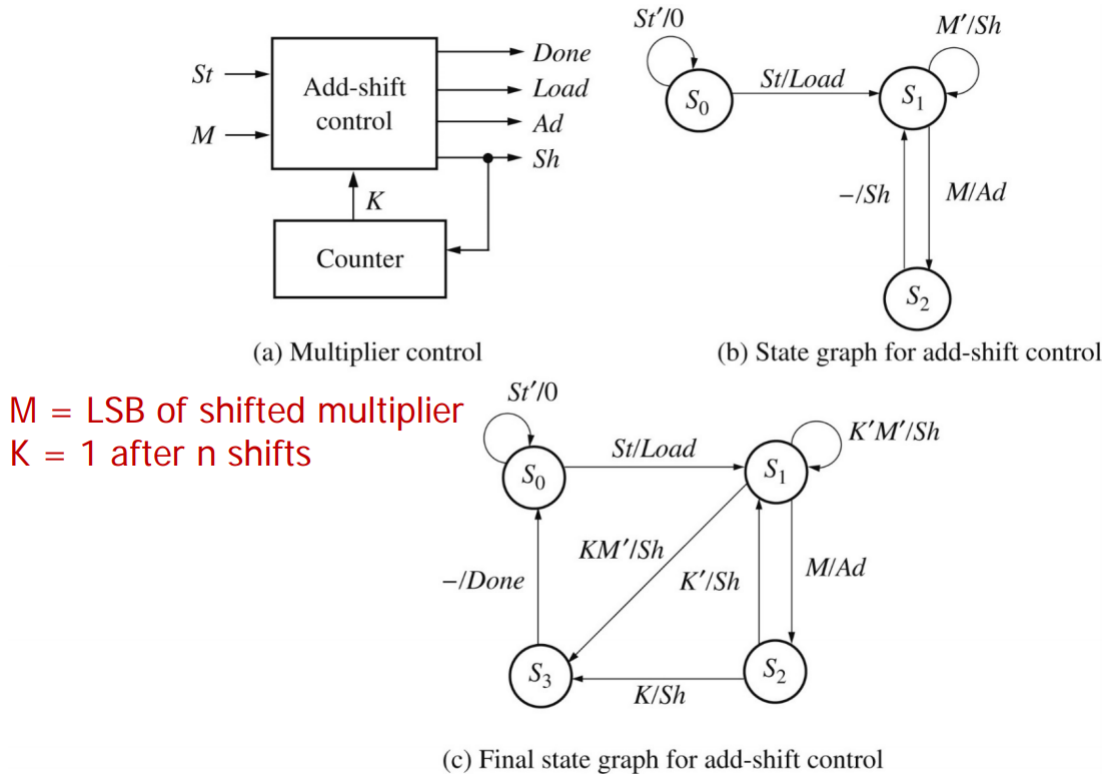


Figure 2: Meele Machine

Time	State	Counter	Product Register	St	M	K	Load	Ad	Sh	Done
$t_0$	$S_0$	00	00000000	0	0	0	0	0	0	0
$t_1$	$S_0$	00	00000000	1	0	0	1	0	0	0
$t_2$	$S_1$	00	000001011	0	1	0	0	1	0	0
$t_3$	$S_2$	00	011011011	0	1	0	0	0	1	0
$t_4$	$S_1$	01	001101101	0	1	0	0	1	0	0
$t_5$	$S_2$	01	100111101	0	1	0	0	0	1	0
$t_6$	$S_1$	10	010011110	0	0	0	0	0	1	0
$t_7$	$S_1$	11	001001111	0	1	1	0	1	0	0
$t_8$	$S_2$	11	100011111	0	1	1	0	0	1	0
$t_9$	$S_3$	00	010001111	0	1	0	0	0	0	1

Figure 3: Stages counter

Time	State	Counter	Product Register	St	M	K	Load	Ad	Sh	Done
$t_0$	$S_0$	00	000000000	0	0	0	0	0	0	0
$t_1$	$S_0$	00	000000000	1	0	0	1	0	0	0
$t_2$	$S_1$	00	000001011	0	1	0	0	1	0	0
$t_3$	$S_2$	00	011011011	0	1	0	0	0	1	0
$t_4$	$S_1$	01	001101101	0	1	0	0	1	0	0
$t_5$	$S_2$	01	100111101	0	1	0	0	0	1	0
$t_6$	$S_1$	10	010011110	0	0	0	0	0	1	0
$t_7$	$S_1$	11	001001111	0	1	1	0	1	0	0
$t_8$	$S_2$	11	100011111	0	1	1	0	0	1	0
$t_9$	$S_3$	00	010001111	0	1	0	0	0	0	1

Figure 4: System Outputs

M	A	Q	CNT	State	
110	0000	101	0	INIT	Multiplicand->M, 0->A, Multiplier->Q, CNT=0
	+ 110			ADD	(Since Q0=1) A = A+M
	0110	101	0		
	0011	010	1	SHIFT	Shift A:Q, CNT+1=1 (CNT not 3 yet)
					(skip ADD, since Q0 = 0)
	0001	101	2	SHIFT	Shift A:Q, CNT+1=2 (CNT not 3 yet)
	+ 110			ADD	(Since Q0 = 1) A = A+M
	0111	101	2		
	0011	110	3	SHIFT	Shift A:Q, CNT+1=2 (CNT= 3)
	0011	110	3	HALT	Done = 1
	<div style="border-top: 1px solid red; width: 100px; margin-top: 5px;"></div> P = 30				

Figure 5: Stages overview

## 2 Software Implementation (VHDL)

The multiplier was designed using Structural VHDL. The multiplier unit consists of a control unit, 3 registers, and an adder. The top level module in section 2.1 highlights the full system, The main objective of this module is to connect the multiplier designed to the 7 segment code.

The seven segment code in section 2.2 works using a clock divider that cycles through the anode activations to display one number at a time. The number displayed is then sent to the appropriate location on the display based on the anodes and the position in the binary representation of the number to be displayed. A decoder is then used to translate the binary representation to the appropriate output for the seven segment display representation.

The multiplier unit takes two 4-line inputs and sends out an 8-line output. The multiplier's algorithm starts when the start signal switches from low to high. The algorithm is complete when done signal is high. The multiplier code in section 2.3 connects the control unit, ALU(adder), and the registers together. The functionality of the code in the section below is described using comments.

## 2.1 Top-Level Module

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TopLevel is
    ---Setting the top level inputs and outputs
    Port ( SW : in STD_LOGIC_VECTOR (15 downto 0);
          LED : out STD_LOGIC_VECTOR (15 downto 0);
          Anodes : out STD_LOGIC_VECTOR (7 downto 0);
          sevenOut : out STD_LOGIC_VECTOR (6 downto 0);
          clock : in STD_LOGIC;
          BTNC : in STD_LOGIC
          );

end TopLevel;

architecture Behavioral of TopLevel is
    ---Inserting the seven segment component
    component sevenSegDriver is
        Port (
            displayed_number: in STD_LOGIC_VECTOR (31 downto 0);
            clock_100Mhz : in STD_LOGIC; -- 100Mhz clock on Basys 3 FPGA board
            reset : in STD_LOGIC; -- reset
            Anode_Activate : out STD_LOGIC_VECTOR (7 downto 0); -- 8 Anode signals
            LED_out : out STD_LOGIC_VECTOR (6 downto 0));
    end component;
    ---Inserting the multiplier component
    component multUnit is
    port (
        MPLIER: in std_logic_vector(3 downto 0);
```



```

    MCAND: in std_logic_vector(3 downto 0);
    result: out std_logic_vector(7 downto 0);
    startSignal: in std_logic;
    clockSignal: in std_logic;
    doneSignal: out std_logic);
end component;
---Signals to be used
signal multout: std_logic_vector(31 downto 0);

begin

    multout(27 downto 24) <= SW(7 downto 4); ---Set switch 4,5,6,and 7 to Multiplier
    multout(19 downto 16) <= SW(3 downto 0); ---Set switch 1,2,3,and 4 to Multiplican

    multiplier: multUnit ---Connecting signals to the multiplier Unit
    port map(SW(7 downto 4), SW(3 downto 0), multout(7 downto 0), BTNC, clock, LED(0));

    sevenSeg: sevenSegDriver ---Connecting signals to the 7 segment
    port map(multout, clock, '0', Anodes, sevenOut);

end Behavioral;

```

## 2.2 7-Segment Display

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_unsigned.all;

entity sevenSegDriver is
    Port (
        displayed_number: in STD_LOGIC_VECTOR (31 downto 0);

        clock_100Mhz : in STD_LOGIC;-- 100Mhz clock
        reset : in STD_LOGIC; -- reset
        Anode_Activate : out STD_LOGIC_VECTOR (7 downto 0);-- 8 Anode signals
        LED_out : out STD_LOGIC_VECTOR (6 downto 0));
end sevenSegDriver;

architecture Behavioral of sevenSegDriver is
    signal LED_BCD: STD_LOGIC_VECTOR (3 downto 0);
    signal refresh_counter: STD_LOGIC_VECTOR (19 downto 0);

```

```

signal LED_activating_counter: std_logic_vector(2 downto 0);

begin

process(LED_BCD)
begin
    case LED_BCD is
        when "0000" => LED_out <= "0000001"; -- "0"
        when "0001" => LED_out <= "1001111"; -- "1"
        when "0010" => LED_out <= "0010010"; -- "2"
        when "0011" => LED_out <= "0000110"; -- "3"
        when "0100" => LED_out <= "1001100"; -- "4"
        when "0101" => LED_out <= "0100100"; -- "5"
        when "0110" => LED_out <= "0100000"; -- "6"
        when "0111" => LED_out <= "0001111"; -- "7"
        when "1000" => LED_out <= "0000000"; -- "8"
        when "1001" => LED_out <= "0000100"; -- "9"
        when "1010" => LED_out <= "0001000"; -- a
        when "1011" => LED_out <= "1100000"; -- b
        when "1100" => LED_out <= "0110001"; -- C
        when "1101" => LED_out <= "1000010"; -- d
        when "1110" => LED_out <= "0110000"; -- E
        when "1111" => LED_out <= "0111000"; -- F
        when others => LED_out <= "0000001";
    end case;
end process;

process(clock_100Mhz,reset)
begin
    if(reset='1') then
        refresh_counter <= (others => '0');
    elsif(rising_edge(clock_100Mhz)) then
        refresh_counter <= refresh_counter + 1;
    end if;
end process;
LED_activating_counter <= refresh_counter(19 downto 17);

process(LED_activating_counter, displayed_number)
begin
    case LED_activating_counter is
        when "000" =>

```

```

        Anode_Activate <= "01111111";
        LED_BCD <= displayed_number(3 downto 0);
when "001" =>
    Anode_Activate <= "10111111";
    LED_BCD <= displayed_number(7 downto 4);
when "010" =>
    Anode_Activate <= "11011111";
    LED_BCD <= displayed_number(11 downto 8);
when "011" =>
    Anode_Activate <= "11101111";
    LED_BCD <= displayed_number(15 downto 12);
when "100" =>
    Anode_Activate <= "11110111";
    LED_BCD <= displayed_number(19 downto 16);
when "101" =>
    Anode_Activate <= "11111011";
    LED_BCD <= displayed_number(23 downto 20);
when "110" =>
    Anode_Activate <= "11111101";
    LED_BCD <= displayed_number(27 downto 24);
when "111" =>
    Anode_Activate <= "11111110";
    LED_BCD <= displayed_number(31 downto 28);
when others => Anode_Activate <="11101111";
end case;
end process;

end Behavioral;

```

## 2.3 Multiplier

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
library xil_defaultlib;
---Declaring Entity of Multiplier Unit
entity multUnit is
port (
    MPLIER: in std_logic_vector(3 downto 0);
    MCAND: in std_logic_vector(3 downto 0);
    result: out std_logic_vector(7 downto 0);
    startSignal: in std_logic;

```

```

    clockSignal: in std_logic;
    doneSignal: out std_logic);
end multUnit;
---Declaring Architecture of Multiplication Unit
architecture Behavioral of multUnit is
    ---Using Component Package
    use xil_defaultlib.componentPackage.all;
    ---Signals used to connect components
    signal regM,regQ: std_logic_vector (3 downto 0); ---Carries output of Register M and Q
    signal regD,regProduct: std_logic_vector (4 downto 0); ---Last bit is a carry bit
    signal loadSignal,shiftSignal,addSignal: std_logic; ---State signals

begin
    ---Porting components
    Control: controlUnit generic map (2)
    port map (clockSignal,regQ(0),startSignal,loadSignal,shiftSignal,addSignal,doneSignal);

    Adder: ALU generic map (4)
    port map (regProduct(3 downto 0),regM,regD);

    MPCReg: multRegister generic map (4)
    port map (MCAND,regM,clockSignal,loadSignal,'0','0','0');

    MPLReg: multRegister generic map (4)
    port map (MPLIER,regQ,clockSignal,loadSignal,shiftSignal,'0',regProduct(0));
    ---Set N to 5 due to carry included in input
    ProdReg: multRegister generic map (5)
    port map (regD,regProduct,clockSignal,addSignal,shiftSignal,loadSignal,'0');
    ---Set result ignore carry
    result <= regProduct(3 downto 0) & regQ;
    ---END OF COMPONENT CONNECTION
end Behavioral;

```

## 2.4 Control Unit

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
---Setting Control Unit inputs and outputs
entity controlUnit is
    generic (N: integer := 2);

```

```

port (
    Clock: in std_logic; ---Clock connection
    LSB: in std_logic; ---Value that contains LSB
    startPulse: in std_logic; ---Start signal
    loadSignal: out std_logic; ---Load signal
    shiftSignal: out std_logic; ---Shift signal
    SignalToA: out std_logic; ---Signal to Product Regg
    Complete: out std_logic --- Done Signal
);
end controlUnit;

architecture Behavioral of controlUnit is
    type states is (waitStage,initStage,sendStage,addStage,shiftStage);
    signal state: states := waitStage;
    signal iterationSignal: unsigned(N-1 downto 0);

begin
    Complete <= '1' when state = waitStage else '0'; ---Terminate the Algorithm
    loadSignal <= '1' when state = initStage else '0'; ---Set load signal if init
    SignalToA <= '1' when state = addStage else '0'; ---Set ALU signal if add
    shiftSignal <= '1' when state = shiftStage else '0'; ---Set shift signal

    process(Clock) ---Run as clock ticks
    begin
        if rising_edge(Clock) then ---At rising edge of clock, set signals
            case state is ---Check State
                when waitStage => if startPulse = '1' then
                    state <= initStage; ---set state to initialization
                end if;

                when initStage => state <= sendStage;
                when sendStage => if (LSB = '1') then
                    state <= addStage; ---set state to addition
                else
                    state <= shiftStage;
                end if;
                when addStage => state <= shiftStage;
                when shiftStage => if (iterationSignal = 2*N - 1) then
                    state <= waitStage; ---Set state to idle
                else
                    state <= sendStage; ---Set state to send signals
            end case;
        end if;
    end process;
end Behavioral;

```

```

        end if;
    end case;
end if;
end process;

process(Clock) ---Count iterations
begin
    if rising_edge(Clock) then
        if state = initStage then
            iterationSignal <= to_unsigned(0,N);
        elsif state = shiftStage then
            iterationSignal <= iterationSignal + 1; ---Increment counter
        end if;
    end if;
end process;

end Behavioral;

```

## 2.5 Registers

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
---Registers used in the multiplication design. The same register implementation
---is used to keep design simple and easy to understand
entity multRegister is
    generic (N: integer := 4);
    port (
        regIn: in std_logic_vector(N-1 downto 0); ---Value to be shifted
        regOut: out std_logic_vector(N-1 downto 0); ---Output of value after shifting
        clock: in std_logic; ---Running the clock to process the register
        LoadEnable: in std_logic; ---Load signal that allows the register to read the regIn value
        shiftEnable: in std_logic; ---Signal that tells register to shift input
        reset: in std_logic; ---reset signal
        SerialInput: in std_logic ---Serial input if register is not in idle mode
    );
end multRegister;

architecture Behavioral of multRegister is
    signal regState: std_logic_vector(N-1 downto 0);
begin
    process (clock) ---Runs the code below as clock ticks

```

```

begin
    if (rising_edge(clock)) then ---On high edge set the registerState Value
        if (reset = '1') then
            regState <= (others => '0'); ---If reset is high reset the value
        elsif (LoadEnable = '1') then
            regState <= regIn; --- Load regIn
        elsif (shiftEnable = '1') then
            regState <= SerialInput & regState(N-1 downto 1); ---Shift register state and
        end if;
    end if;
end process;
regOut <= regState; ---Set register output to regState

end Behavioral;

```

## 2.6 Component Package

```

library ieee;
use ieee.std_logic_1164.all;

package componentPackage is
    ---Declaring Control Unit
    component controlUnit
        generic (N: integer := 2);
        port (
            Clock: in std_logic;
            LSB: in std_logic;
            startPulse: in std_logic;
            loadSignal: out std_logic;
            shiftSignal: out std_logic;
            SignalToA: out std_logic;
            Complete: out std_logic
        );
    end component;
    ---Declaring ALU
    component ALU
        generic (N: integer := 4);
        port(
            in1: in std_logic_vector(N-1 downto 0);
            in2: in std_logic_vector(N-1 downto 0);
            output: out std_logic_vector(N downto 0)
        );
    end component;
end package componentPackage;

```

```

);
end component;
---Declaring Registers
component multRegister is
generic (N: integer := 4);
port (
    regIn: in std_logic_vector(N-1 downto 0);
    regOut: out std_logic_vector(N-1 downto 0);
    clock: in std_logic;
    LoadEnable: in std_logic;
    shiftEnable: in std_logic;
    reset: in std_logic;
    SerialInput: in std_logic
);
end component;
---END OF PACKAGE
end package;

```

## 2.7 Bench Test

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity testMultTop is
end testMultTop;

architecture Behavioral of testMultTop is
    component multUnit is
    port (
        MPLIER: in std_logic_vector(3 downto 0);
        MCAND: in std_logic_vector(3 downto 0);
        result: out std_logic_vector(7 downto 0);
        startSignal: in std_logic;
        ClockSignal: in std_logic;
        doneSignal: out std_logic);
    end component;

    signal MPLIER: std_logic_vector(3 downto 0);
    signal MCAND: std_logic_vector(3 downto 0);
    signal result: std_logic_vector(7 downto 0);

```



```

signal startSignal: std_logic:= '0';
signal ClockSignal: std_logic;
signal doneSignal: std_logic;

component binary_multiplier
port(
    CLK, RESET, G, LOADB, LOADQ: in std_logic;
    MULT_IN: in std_logic_vector(3 downto 0);
    MULT_OUT: out std_logic_vector(7 downto 0));
end component;

signal CLK, RESET, G, LOADB, LOADQ: std_logic;
signal MULT_IN: std_logic_vector(3 downto 0);
signal MULT_OUT: std_logic_vector(7 downto 0);

begin
    uut: multUnit
        port map(
            MPLIER => MPLIER,
            MCAND => MCAND,
            result => result,
            startSignal => startSignal,
            ClockSignal => ClockSignal,
            doneSignal => doneSignal
        );

    uut1: binary_multiplier
        port map(
            CLK => Clk,
            RESET => RESET,
            G => G,
            LOADB => LOADB,
            LOADQ => LOADQ,
            MULT_IN => MULT_IN,
            MULT_OUT => MULT_OUT
        );

    clk_process :process
begin

```

```

        ClockSignal <= '0';
        CLK <= '0';
        wait for 10ns;
        ClockSignal <= '1';
        CLK <= '1';
        wait for 10ns;
    end process;

stim_proc:
    process
    begin

        MPLIER <= std_logic_vector(to_unsigned(4,4));
        MCAND <= std_logic_vector(to_unsigned(6,4));

        startSignal <= '0', '1' after 5 ns, '0' after 40 ns;

        wait until doneSignal = '1';

        wait for 5ns;

        LOADB <= '0';
        LOADQ <= '0';
        wait for 50 ns;
        MULT_IN <= std_logic_vector(to_unsigned(6,4));
        LOADB <= '1';
        wait for 50 ns;
        LOADB <= '0';
        MULT_IN <= std_logic_vector(to_unsigned(4,4));
        LOADQ <= '1';
        wait for 50ns;
        LOADQ <= '0';
        G <= '1';

        end process;
end Behavioral;

```

## 2.8 Top ALU

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
---Setting the entity of the nBit ALU
entity nBitAlu is
    generic (
        N : integer := 8    ---Building a 4 Bit ALU
    );
    port (
        in1, in2 : in std_logic_vector(N - 1 downto 0);    ---4 inputs and 3 outputs
        output : out std_logic_vector(N - 1 downto 0)
    );
end nBitAlu;
---Setting Architecture of N bit ALU
architecture Structural of nBitAlu is
    ---Using the ALU designed previously
    component ALU
        Port ( in1 : in  std_logic;
              in2 : in  std_logic;
              sel : in  STD_LOGIC_vector(1 downto 0);
              cin : in  STD_LOGIC;
              Alu_out : out std_logic;
              cout : out  STD_LOGIC);
    end component;
    ---Setting a 5 signal lines to connect the carries
    signal tempFour: std_logic_vector(N downto 0);
    ---Always run this code below. Code will generate n ALUs
begin
    tempFour(0) <= Cin; ---Setting up the first carry to the first signal line

    GEN_ALU: ---Generating Function
    for i in 0 to N - 1 generate
        nALUDesign : ALU ---4 ALUs are generated here
        port map (in1(i), in2(i), sel, tempFour(i), Alu_out(i) ,tempFour(i+1));
        ---Connecting the ALUs together
    end generate GEN_ALU;

    OVF <= tempFour(N-2) xor tempFour(N-1); ---Generating overflow signal
    process (in1,in2)
    begin

```

```

        if in1 = in2 then ---Generating a zero signal
            zero <= '1';
        else
            zero <= '0';
        end if;
    end process; ---End Process
end Structural;

```

## 2.9 ALU

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
---Setting inputs and outputs
entity ALU is
    Port ( in1 : in  std_logic;
           in2 : in  std_logic;
           sel : in  STD_LOGIC_vector(1 downto 0);
           cin : in  STD_LOGIC;
           Alu_out : out std_logic;
           cout : out  STD_LOGIC);
end ALU;

architecture Structural of ALU is
    ---Declaring Component BitAdder to use in ALU
    component bitAdder
        port (
            in1, in2 : in std_logic;
            mode : in std_logic;
            adder_out : out std_logic;
            carryOutAdder : out std_logic
        );
    end component;
    ---Signals used to connect inputs and outputs to gates
    signal a: std_logic;
    signal b: std_logic;
    signal carryIn: STD_LOGIC := '0';
    ---If sel, In1, In2, or Carryin is high run the ALU
begin
    process(sel, in1, in2, cin)
    begin
        case sel is

```

```

when "00" => ---When sel is 00 carry takes care of both cases
    a <= in1;
    b <= in2;
    carryIn <= cin; ---Carry = 0 (Add A+B) || Carry = 1 (A + comp(B) + 1)
when "01" =>
    if(cin = '0') then --comp(A) + B
        a <= not(in1); ---Compliment in1
        b <= in2;
        carryIn <= cin;
    else
        a <= not(in1); ---comp(A) + comp(-B) + 1
        b <= not(in2); ---comp(B)
        carryIn <= cin; -----Add A-B
    end if;
when "10" =>
    if(cin = '0') then
        a <= in1; ---Sets A to as is
        b <= '1'; ---Sets B to 1
        carryIn <= '1'; ---Add A-B
    else
        a <= in1; ---Send A as it is
        b <= '1'; ---sets B to 1
        carryIn <= '0'; ---Add A+B
    end if;
when "11" =>
    if(cin = '0') then
        a <= not(in1); ---Finds compliment of A
        b <= '0'; ---Set B = 0
        carryIn <= '0'; ---Add A+B
    else
        a <= not(in1); ---Finds compliment of A
        b <= '1'; ---Set B to 1
        carryIn <= '0'; ---Add A+B
    end if;
when others => ---Testing/Debugging
    a <= '0';
    b <= '0';
    carryIn <= '0';

end case;
end process;
BitALU: bitAdder

```

```
port map(a,b,carryIn,Alu_out,cout);
```

```
end Structural;
```

## 2.10 Full Adder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
---Setting inputs and outputs
entity fullAdder is
    Port ( CarryIn : in STD_LOGIC;
          P : in STD_LOGIC;
          Q : in STD_LOGIC;
          SUM : out STD_LOGIC;
          CarryOut : out STD_LOGIC);
end fullAdder;

architecture Structural of fullAdder is
    ---Using the half adder to create a full adder
    Component halfAdder
        Port ( Ain : in STD_LOGIC;
              Bin : in STD_LOGIC;
              AdderOut : out STD_LOGIC;
              carry : out STD_LOGIC);
    end component;
    ---Setting signals to from carryout of half adder to an or gate
    signal CarryToOr1: STD_LOGIC;
    signal CarryToOr2: STD_LOGIC;
    signal SumToQ: STD_LOGIC;
    ---Connecting signals and inputs to 2 half adders
    begin
        HA1: halfAdder
            port map(CarryIn, SumToQ, SUM, CarryToOr1);

        HA2: halfAdder
            port map(P,Q,SumToQ,CarryToOr2);

        CarryOut <= CarryToOr1 or CarryToOr2;
    end Structural;
```

## 2.11 Half Adder

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity halfAdder is
    --- Input to half adder
    Port (  Ain : in STD_LOGIC;
           Bin : in STD_LOGIC;
           AdderOut : out STD_LOGIC;
           carry : out STD_LOGIC);
end halfAdder;

architecture Behavioral of halfAdder is
    ---Design of half Adder
begin
    AdderOut <= Ain xor Bin; ---Input A is XOed with Input B.
    carry <= Ain and Bin;    ---Input A is anded with Input B.

end Behavioral;

```

## 2.12 XDC

```

## Clock signal
set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 } [get_ports { clock }];
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {clock}];

##Switches
set_property -dict { PACKAGE_PIN J15      IOSTANDARD LVCMOS33 } [get_ports { SW[0] }];
set_property -dict { PACKAGE_PIN L16      IOSTANDARD LVCMOS33 } [get_ports { SW[1] }];
set_property -dict { PACKAGE_PIN M13      IOSTANDARD LVCMOS33 } [get_ports { SW[2] }];
set_property -dict { PACKAGE_PIN R15      IOSTANDARD LVCMOS33 } [get_ports { SW[3] }];
set_property -dict { PACKAGE_PIN R17      IOSTANDARD LVCMOS33 } [get_ports { SW[4] }];
set_property -dict { PACKAGE_PIN T18      IOSTANDARD LVCMOS33 } [get_ports { SW[5] }];
set_property -dict { PACKAGE_PIN U18      IOSTANDARD LVCMOS33 } [get_ports { SW[6] }];
set_property -dict { PACKAGE_PIN R13      IOSTANDARD LVCMOS33 } [get_ports { SW[7] }];
set_property -dict { PACKAGE_PIN T8       IOSTANDARD LVCMOS18 } [get_ports { SW[8] }];
set_property -dict { PACKAGE_PIN U8       IOSTANDARD LVCMOS18 } [get_ports { SW[9] }];
set_property -dict { PACKAGE_PIN R16      IOSTANDARD LVCMOS33 } [get_ports { SW[10] }];
set_property -dict { PACKAGE_PIN T13      IOSTANDARD LVCMOS33 } [get_ports { SW[11] }];

```

```

set_property -dict { PACKAGE_PIN H6      IOSTANDARD LVCMOS33 } [get_ports { SW[12] }];
set_property -dict { PACKAGE_PIN U12     IOSTANDARD LVCMOS33 } [get_ports { SW[13] }];
set_property -dict { PACKAGE_PIN U11     IOSTANDARD LVCMOS33 } [get_ports { SW[14] }];
set_property -dict { PACKAGE_PIN V10     IOSTANDARD LVCMOS33 } [get_ports { SW[15] }];

## LEDs
set_property -dict { PACKAGE_PIN H17     IOSTANDARD LVCMOS33 } [get_ports { LED[0] }];
set_property -dict { PACKAGE_PIN K15     IOSTANDARD LVCMOS33 } [get_ports { LED[1] }];
set_property -dict { PACKAGE_PIN J13     IOSTANDARD LVCMOS33 } [get_ports { LED[2] }];
set_property -dict { PACKAGE_PIN N14     IOSTANDARD LVCMOS33 } [get_ports { LED[3] }];
set_property -dict { PACKAGE_PIN R18     IOSTANDARD LVCMOS33 } [get_ports { LED[4] }];
set_property -dict { PACKAGE_PIN V17     IOSTANDARD LVCMOS33 } [get_ports { LED[5] }];
set_property -dict { PACKAGE_PIN U17     IOSTANDARD LVCMOS33 } [get_ports { LED[6] }];
set_property -dict { PACKAGE_PIN U16     IOSTANDARD LVCMOS33 } [get_ports { LED[7] }];
set_property -dict { PACKAGE_PIN V16     IOSTANDARD LVCMOS33 } [get_ports { LED[8] }];
set_property -dict { PACKAGE_PIN T15     IOSTANDARD LVCMOS33 } [get_ports { LED[9] }];
set_property -dict { PACKAGE_PIN U14     IOSTANDARD LVCMOS33 } [get_ports { LED[10] }];
set_property -dict { PACKAGE_PIN T16     IOSTANDARD LVCMOS33 } [get_ports { LED[11] }];
set_property -dict { PACKAGE_PIN V15     IOSTANDARD LVCMOS33 } [get_ports { LED[12] }];
set_property -dict { PACKAGE_PIN V14     IOSTANDARD LVCMOS33 } [get_ports { LED[13] }];
set_property -dict { PACKAGE_PIN V12     IOSTANDARD LVCMOS33 } [get_ports { LED[14] }];
set_property -dict { PACKAGE_PIN V11     IOSTANDARD LVCMOS33 } [get_ports { LED[15] }];

##7 segment display
set_property -dict { PACKAGE_PIN T10     IOSTANDARD LVCMOS33 } [get_ports { sevenOut[6] }];
set_property -dict { PACKAGE_PIN R10     IOSTANDARD LVCMOS33 } [get_ports { sevenOut[5] }];
set_property -dict { PACKAGE_PIN K16     IOSTANDARD LVCMOS33 } [get_ports { sevenOut[4] }];
set_property -dict { PACKAGE_PIN K13     IOSTANDARD LVCMOS33 } [get_ports { sevenOut[3] }];
set_property -dict { PACKAGE_PIN P15     IOSTANDARD LVCMOS33 } [get_ports { sevenOut[2] }];
set_property -dict { PACKAGE_PIN T11     IOSTANDARD LVCMOS33 } [get_ports { sevenOut[1] }];
set_property -dict { PACKAGE_PIN L18     IOSTANDARD LVCMOS33 } [get_ports { sevenOut[0] }];
set_property -dict { PACKAGE_PIN J17     IOSTANDARD LVCMOS33 } [get_ports { Anodes[7] }];
set_property -dict { PACKAGE_PIN J18     IOSTANDARD LVCMOS33 } [get_ports { Anodes[6] }];
set_property -dict { PACKAGE_PIN T9      IOSTANDARD LVCMOS33 } [get_ports { Anodes[5] }];
set_property -dict { PACKAGE_PIN J14     IOSTANDARD LVCMOS33 } [get_ports { Anodes[4] }];
set_property -dict { PACKAGE_PIN P14     IOSTANDARD LVCMOS33 } [get_ports { Anodes[3] }];
set_property -dict { PACKAGE_PIN T14     IOSTANDARD LVCMOS33 } [get_ports { Anodes[2] }];
set_property -dict { PACKAGE_PIN K2      IOSTANDARD LVCMOS33 } [get_ports { Anodes[1] }];
set_property -dict { PACKAGE_PIN U13     IOSTANDARD LVCMOS33 } [get_ports { Anodes[0] }];

##Buttons
#set_property -dict { PACKAGE_PIN C12     IOSTANDARD LVCMOS33 } [get_ports { CPU_RESETN }];
set_property -dict { PACKAGE_PIN N17     IOSTANDARD LVCMOS33 } [get_ports { BTNC }];

```



```
#set_property -dict { PACKAGE_PIN M18    IOSTANDARD LVCMOS33 } [get_ports { BTNU }];
#set_property -dict { PACKAGE_PIN P17    IOSTANDARD LVCMOS33 } [get_ports { BTNL }];
#set_property -dict { PACKAGE_PIN M17    IOSTANDARD LVCMOS33 } [get_ports { BTNR }];
#set_property -dict { PACKAGE_PIN P18    IOSTANDARD LVCMOS33 } [get_ports { BTND }];
```

### 3 Hardware Overview

#### 3.1 Hardware Implementation

Multiplier hardware consists of a control unit designed using sequential decoders and registers to keep track of what stage the algorithm is currently in. The structural ALU designed in Lab 2 was used in the design. The structural ALU consists of a full adder cascaded to form a 4 bit adder. The hardware schematic is described in section 3.2. Figure 1 describes the hardware schematic of the top level program. The top level consists of the multiplier unit and the seven segment. Figure 2 describes the hardware schematic of the seven segment module. Figure 3 describes the overview of the multiplier unit. The multiplier unit consists of the control unit, registers and the ALU.

#### 3.2 Hardware Schematic

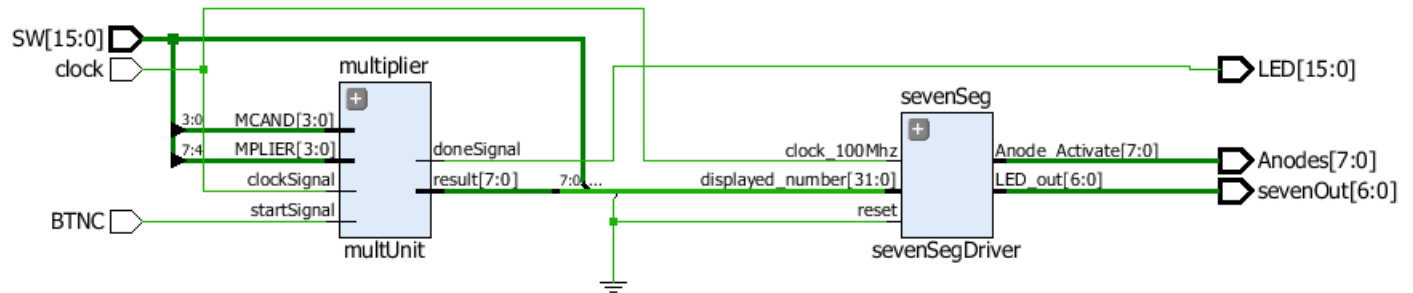


Figure 6: Schematic of the top level module

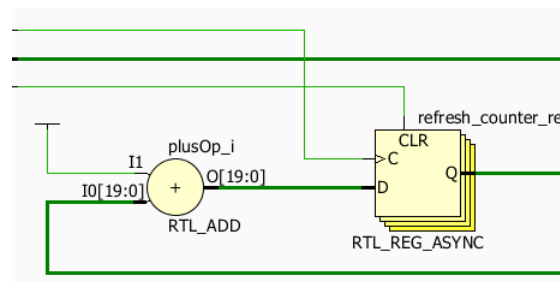


Figure 7: Schematic of the seven segment driver-1

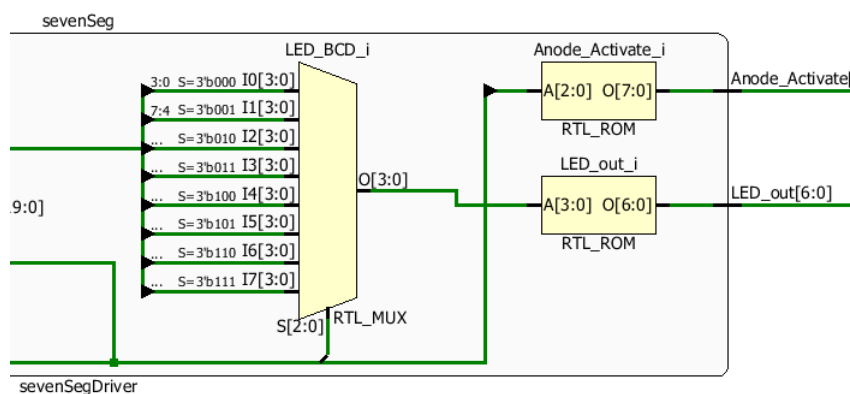


Figure 8: Schematic of the seven segment driver-2

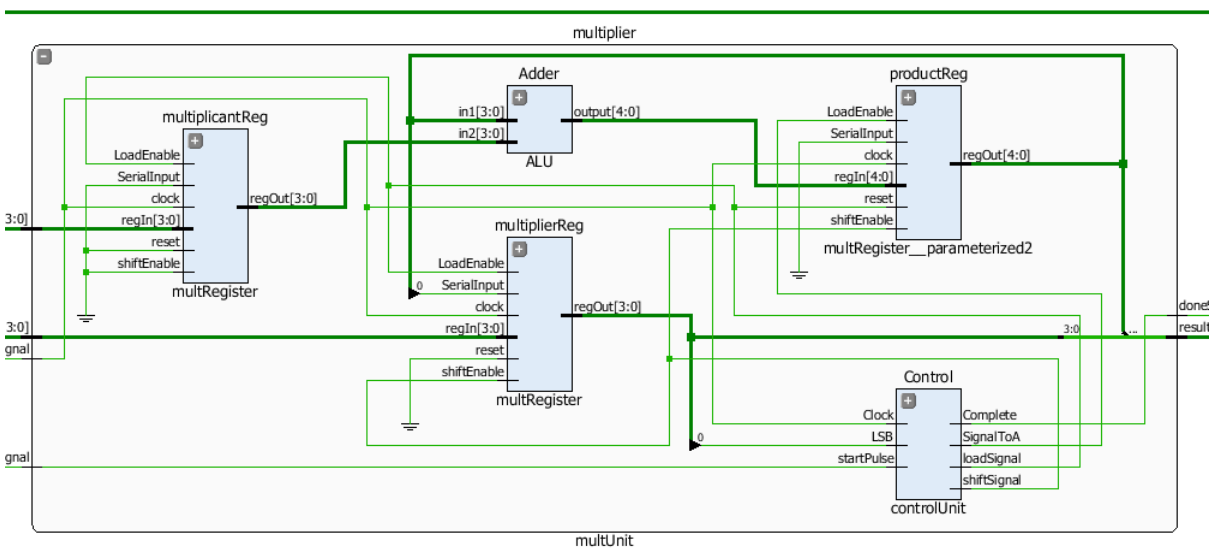


Figure 9: Multiplier Hardware Overview

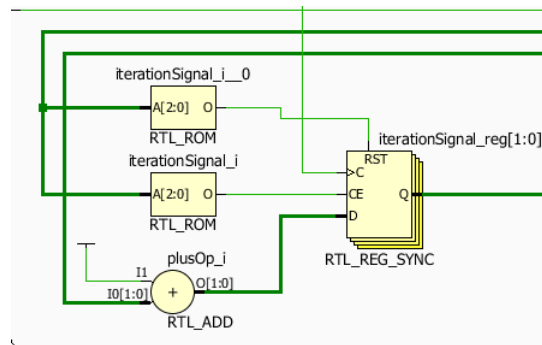


Figure 10: Control Unit Implementation-1

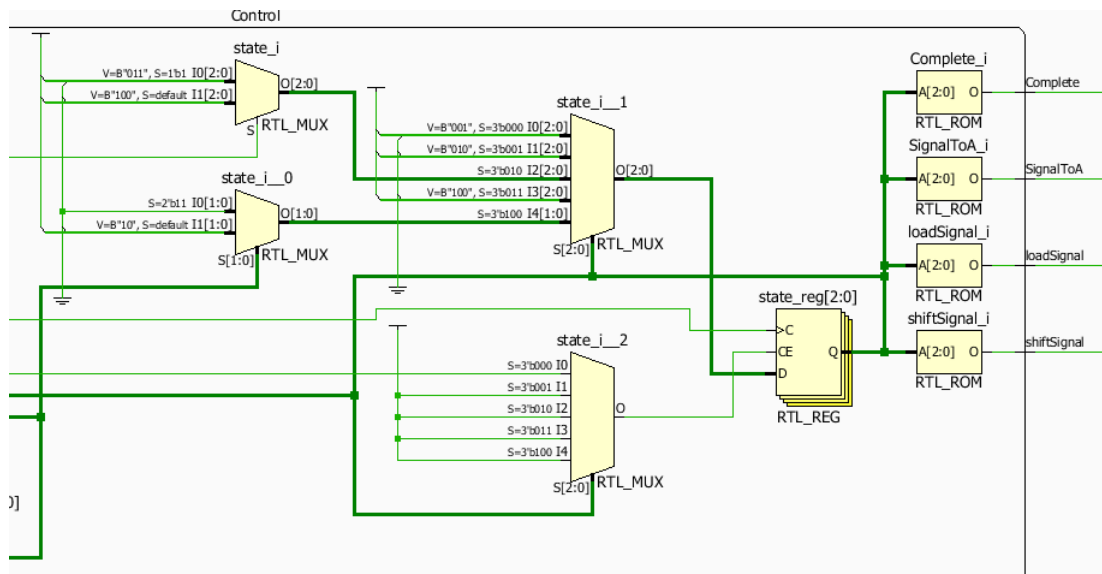


Figure 11: Control Unit Implementation-2

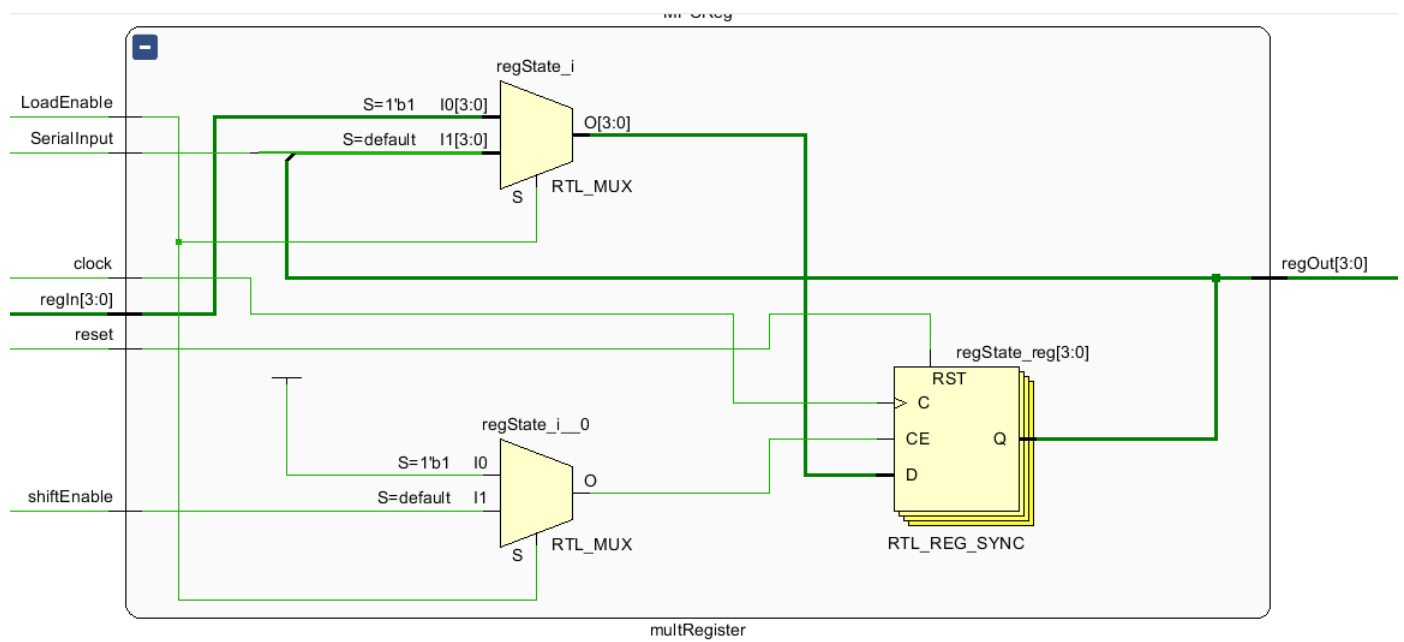


Figure 12: Registers Implementation

3.3 Resources Used

Name	^ 1	Slice LUTs (63400)	Slice Registers (126800)	Slice (15850)	LUT as Logic (63400)	LUT Flip Flop Pairs (63400)	Bonded IOB (210)	BUFGCTRL (32)	
TopLevel		35	40	17	35	17	41	1	
multiplier (multUnit)		20	20	9	20	16	0	0	
sevenSeg (sevenSegDriver)		15	20	13	15	1	0	0	

Figure 13: Resources used summary

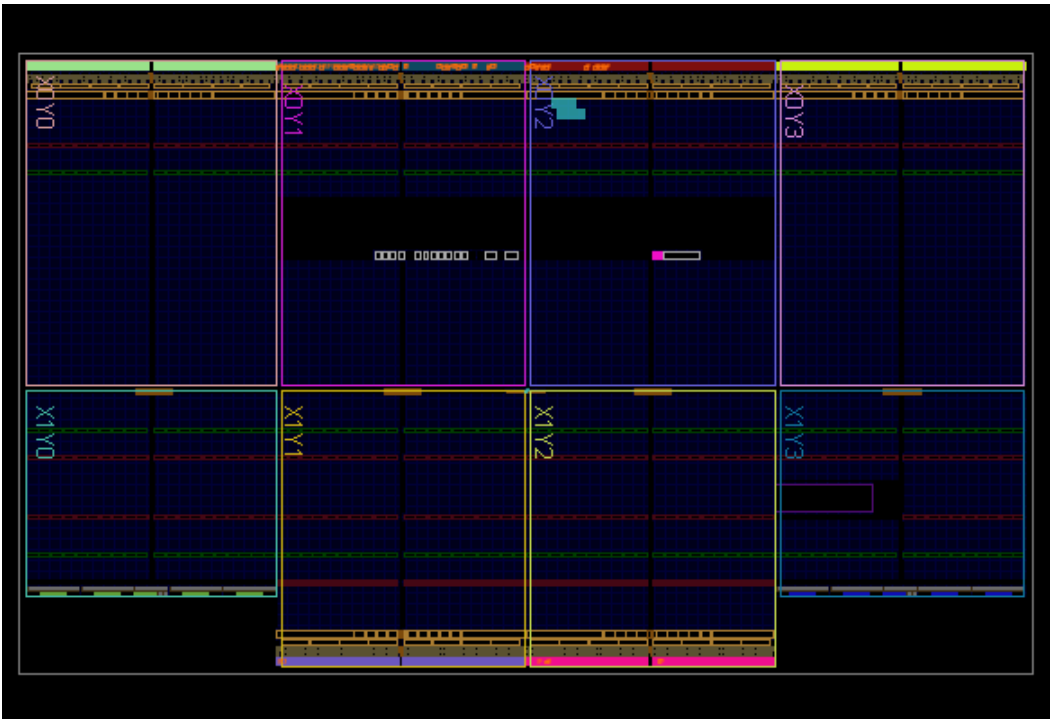


Figure 14: Resources Used from FPGA Board

 


Figure 15: Hardware Usage(Detailed View)

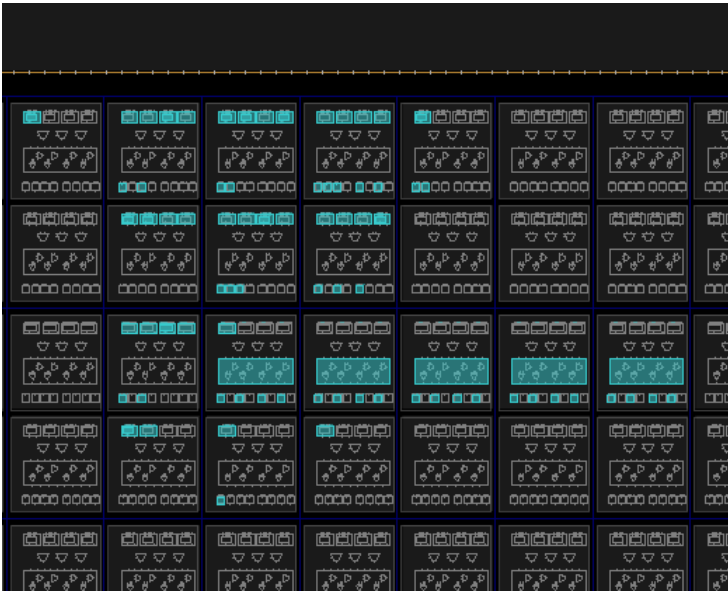


Figure 16: Hardware Usage(Zoomed In View)

## 4 Project Development Process

### 4.1 Error Analysis

When designing the system the first time, a lot of errors were encountered as no clock signal was inputted. The design process had to be restarted. A project development plan was created (Highlighted in section 4). After gaining a deep understanding of the system, the system was easier to re-design. No error in functionality was encountered. Design was successful after second design attempt. By reviewing the simulation wave forms after the design, it was safe to assume that the multiplier produces the expected results. There were no errors in the design or output of the multiplier.

### 4.2 Simulation Analysis

#### 4.2.1 Results Analysis

The results obtained from our design match the expected output exactly, including the shifting of the register from 4 to 2 to 1 to 61 etc. The program uses very little resources as it is extremely small and simple in comparison to the board that is being used. Figure 13 summarizes the resources used.

The simulations below show the functionality of the multipliers in both structural and behavioural designs. Figure 19 displays outputs from both designs for comparison. The speed of the behavioural multiplier is 195ns and the speed of the structural multiplier is 200 ns. The behavioural is faster due to it making use of background processes that were not utilized in the structural implementation. The structural implementation has a doneSignal that is triggered when the multiplication is complete. The value that goes into the shift register starts at 4 and is shifted to 2, 1, then 61. 61 is displayed due to the combination of the highest bits of the product with the lowest bits register Q.

#### 4.2.2 Simulation Figures

 


Figure 17: Structural Implementation Results



 


Figure 18: Behavioral Implementation Results

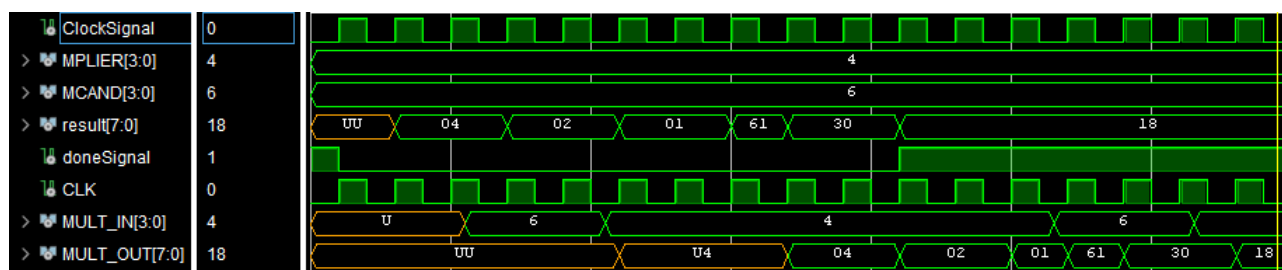


Figure 19: Structural vs Behavioral Comparison

 


Figure 20: Structural Implementation Test 1

 


Figure 21: Structural Implementation Test 2